

Bluetooth RC car

Components

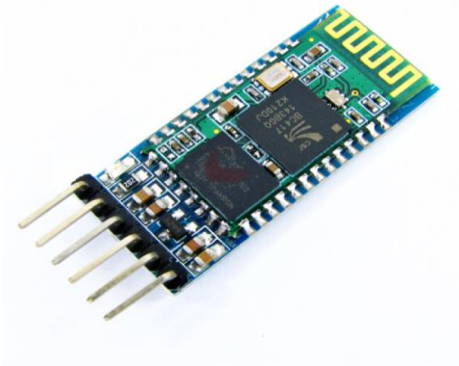- HC-05 Bluetooth transceiver module
- L298N motor driver module
- DC motors and wheels x2
- Batteris ~12 Volt




HC-05

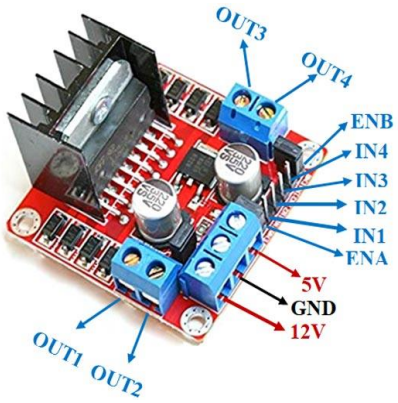


L298N




Circuit diagram

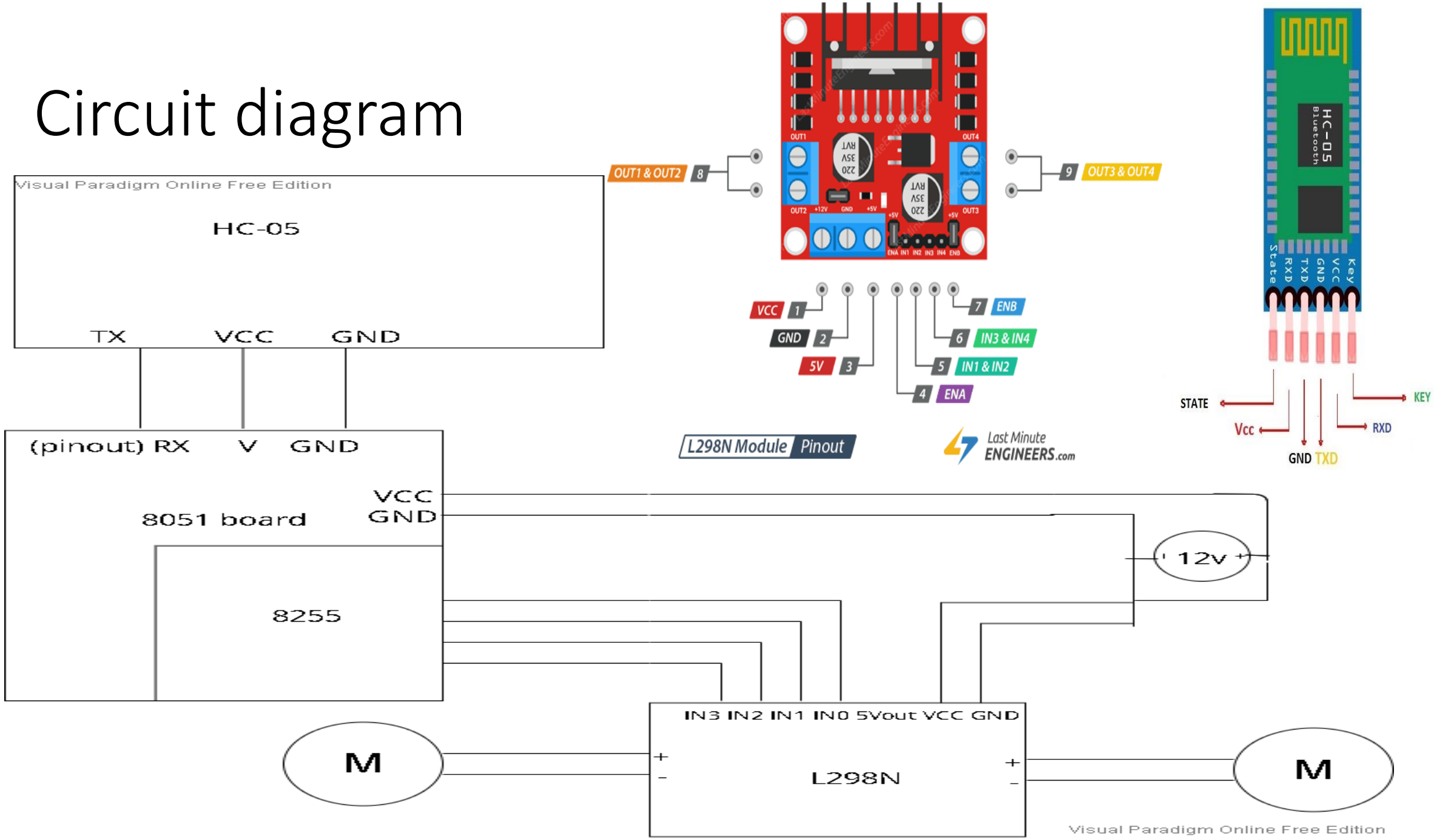

Implementation (1/3): 8051

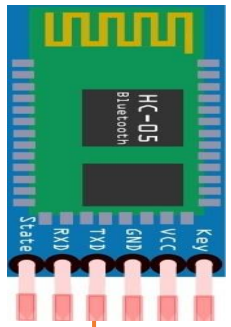


Connect TX of HC-05
To RX of 8051

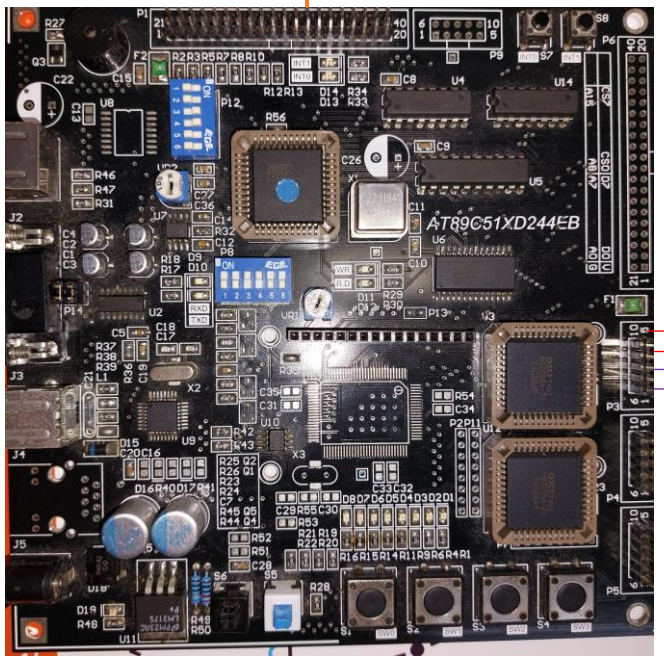

PA.0 PA.1 control
Motor A

PA.2 PA.3 control
Motor B

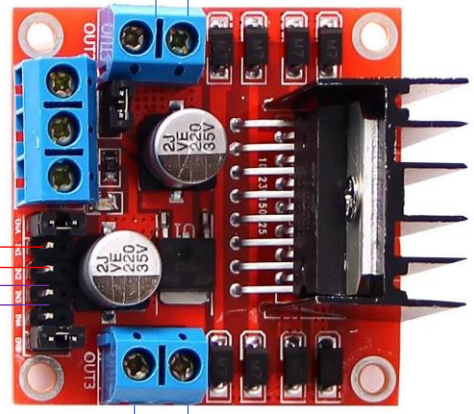

MOTOR A

MOTOR B


HC-05 will receive signal from mobile device and pass to 8051 through serial port.

The signal will then be sent out of the port A of 8255 directly to the input pins of L298N.


Implementation (2/3): mobile


L298N Motor Controller Truth Table			
ENA	**IN1**	**IN2**	**Description**
0	N/A	N/A	Motor A is off
1	0	0	Motor A is stopped (brakes)
1	0	1	Motor A is on and turning backwards
1	1	0	Motor A is on and turning forwards
1	1	1	Motor A is stopped (brakes)

Download from
Google Play Store

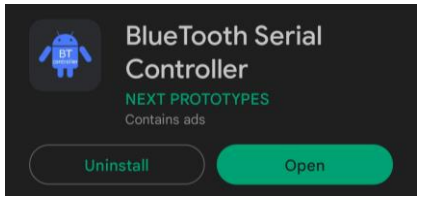

IN1, IN2: MOTOR A
IN3, IN4: MOTOR B

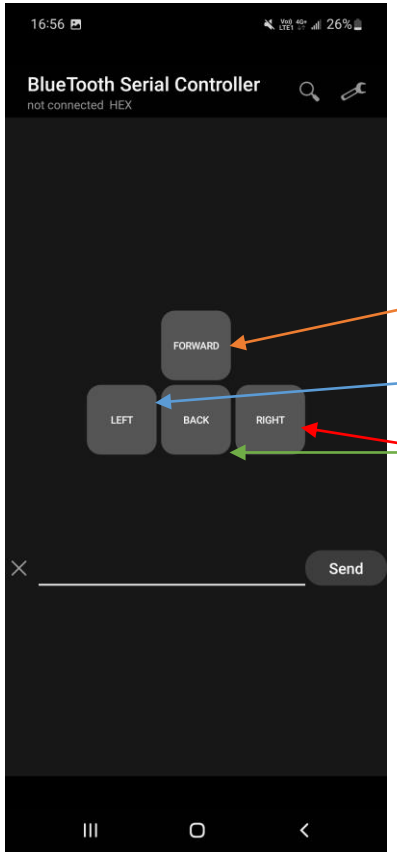

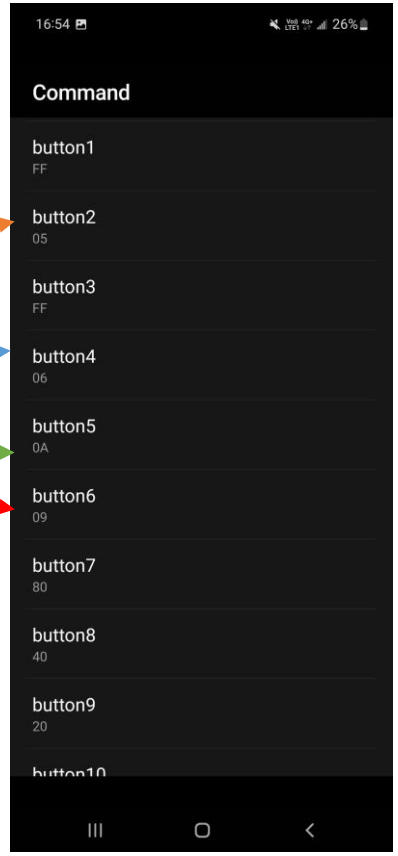

00000101

00000110

00001010

00001001

Implementation (3/3): example

Ex. Turn right

